

ElecSoc Soldering Practice Card

JayceDesign

August 2024

1 Introduction

The practice card is an oscillating circuit with a 555 timer. It blinks 2 sets of LEDs. The oscillating period is controlled with an RC circuit.

2 Assembling the board

The board has 2 sets of components. Required and optional components. The required components are the minimum components needed to assemble to have a working card. The optional components are for soldering practice and to change the oscillator circuit. The required components are marked with an asterisk in the board.

To assemble the card, start with the bigger packages first. There are 4 different packages: 1206, 0805, 0603 and 0402. The bigger the number, the bigger the component, and easier to solder it will be. Start with the practice components first. Assemble first the optional 1206 resistors, then the 0805 LEDs. Then, move on to the practice network on the bottom left of the card. Then, start placing on the required components, from the largest package to the smallest. Lastly, solder on the 555 timer and the pin headers on the left.

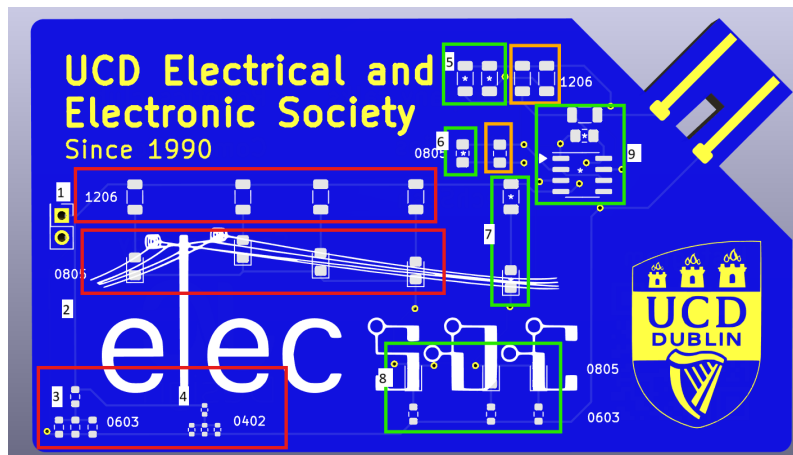


Figure 1: The order of soldering is indicated above.

In red, the practice components. Green, components to assemble once comfortable with the process. Orange, extra components for tuning oscillating circuit. You don't need to solder all optional components, only as many as you need to feel comfortable with the soldering process.

3 Testing

If properly assembled, when the card is powered, the LEDs will blink with a period of 1.5s. The practice network is a voltage divider. The voltage drop at the lower resistors should be 1.25V.

If you add the 5Ω resistor on the top right, you can slot the card in a USB port.

You can add the optional resistors for the oscillator circuit. This will reduce the period to about 0.8s. Adding only the extra capacitor will increase the period to 3.3s.